

Principles and Applications of Microcontrollers

Yan-Fu Kuo

Dept. of Bio-industrial Mechatronics Engineering
National Taiwan University


Today:

- Arduino serial
- Arduino analog I/O
- DC motor control




Quiz

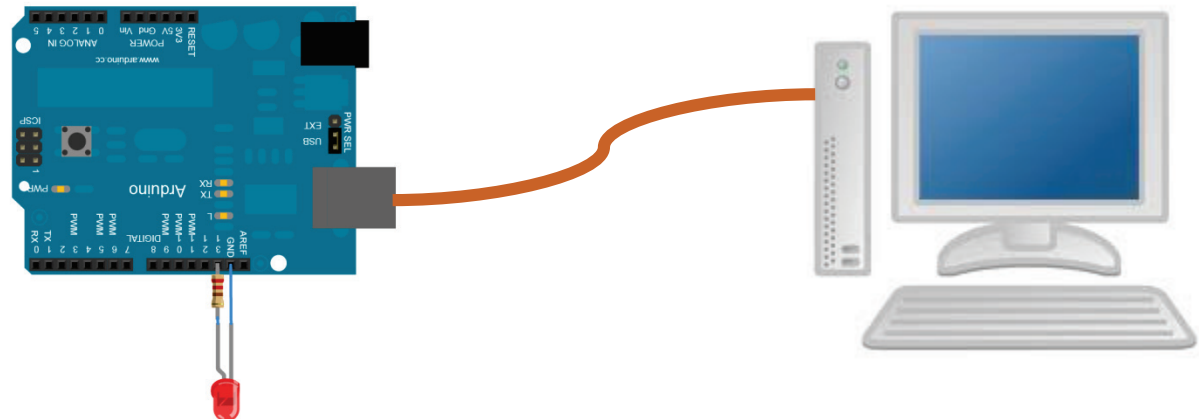- Connect the Arduino to a computer
- Blink the LED at
 - 2Hz when the key 'a'
 - $\frac{1}{2}$ Hz when the key 'b'
 - $\frac{1}{8}$ Hz when the key 'c'of the computer keyboard is pressed
- Turn of the LED if the key 'd' of the computer keyboard is pressed






Direct Current (DC) Motor

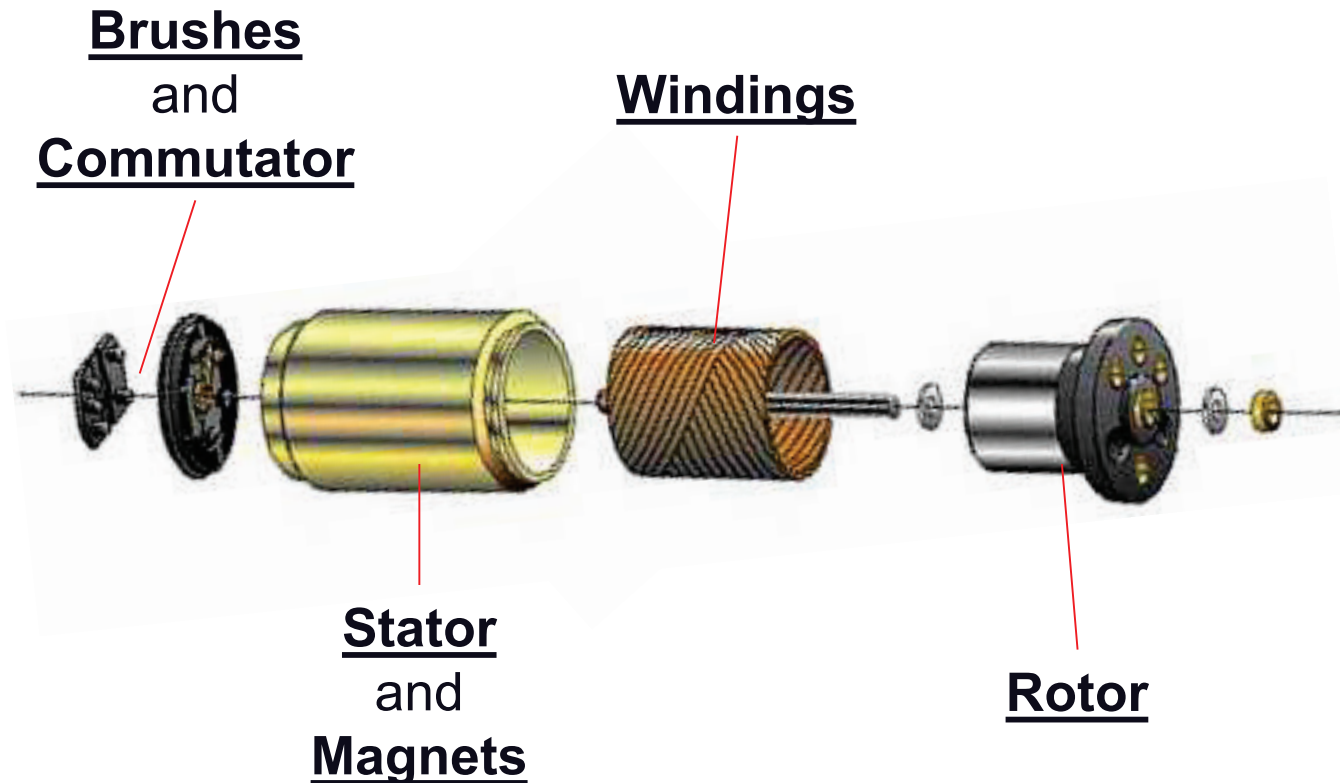


Working Principle of DC Motors

- Follows the Fleming's left-hand rule

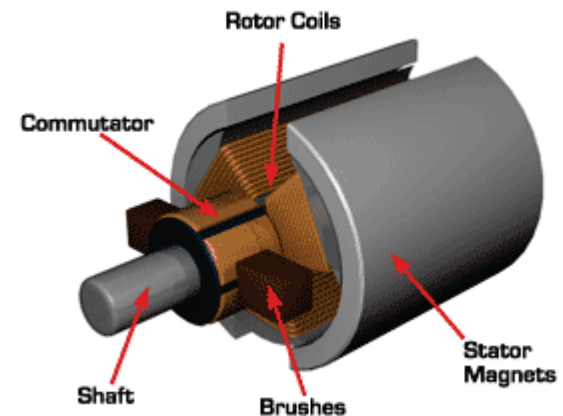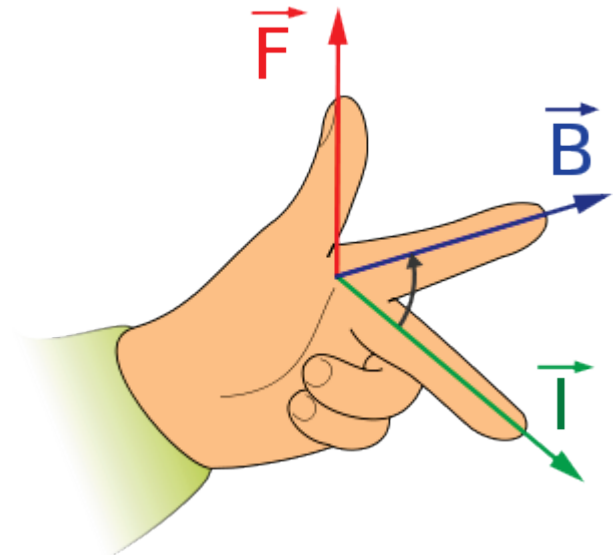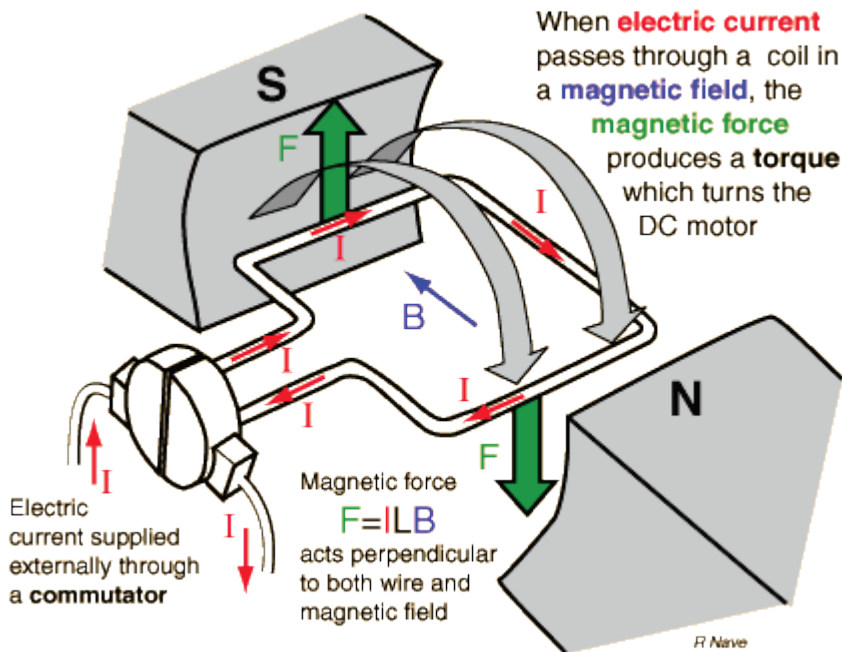

Drive A DC Motor

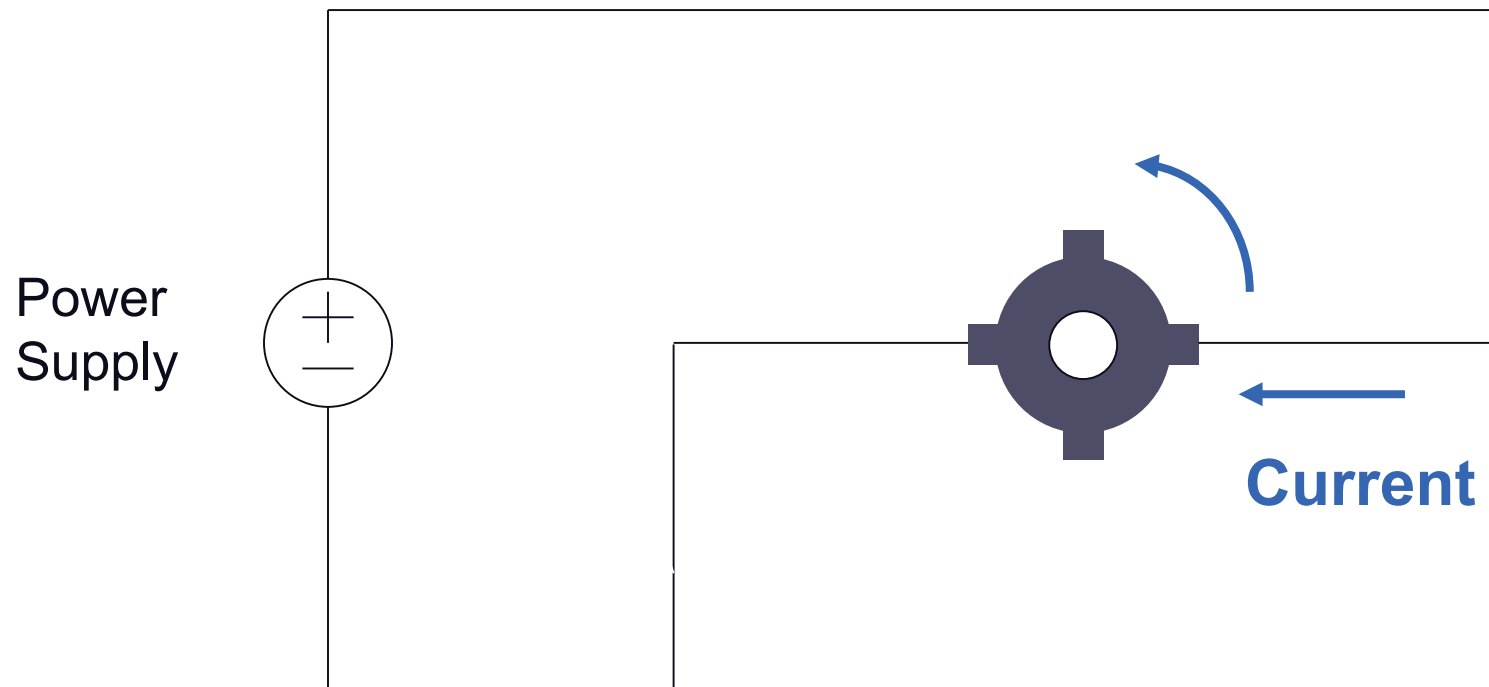- The motor rotates when a voltage is applied to it




- What is the minimum current to drive the DC motor?

Drive A DC Motor Using A MCU?


- Can one drive a DC motor by just wiring it to a MCU?
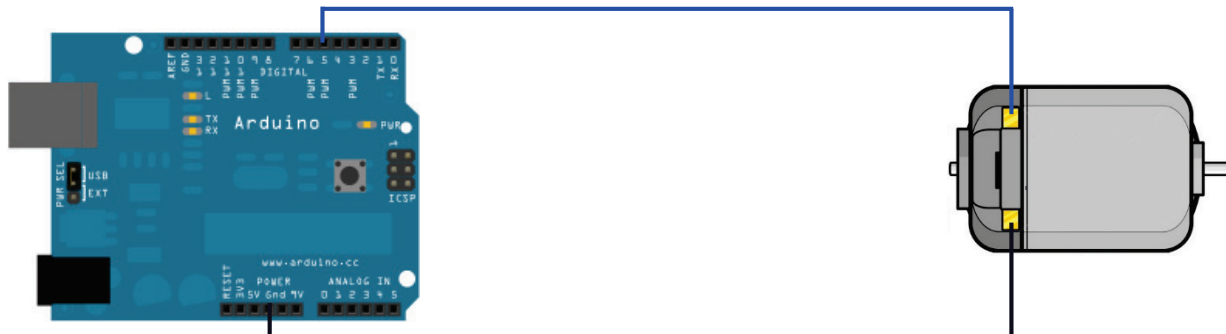
```
int motor = 5;  
void setup() {  
  pinMode(motor, OUTPUT);  
}  
void loop() {  
  digitalWrite(motor, HIGH);  
  delay(4000);  
  digitalWrite(motor, LOW);  
  delay(4000);  
}
```




Bipolar Junction Transistor (BJT)

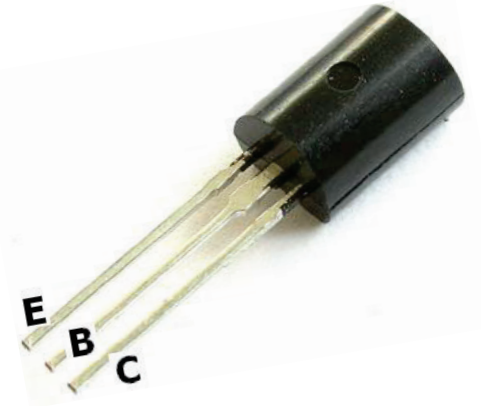
- Three-terminal semiconductor device
- Can perform switching: controlling a relative large current between or voltage across two terminals using a small control current or voltage



NPN

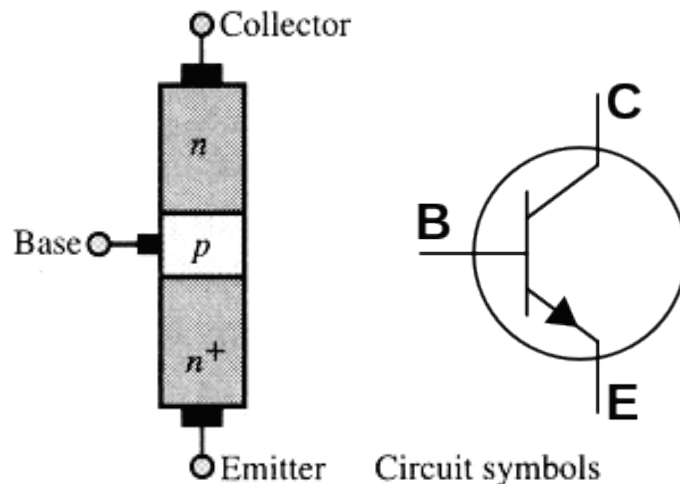


PNP

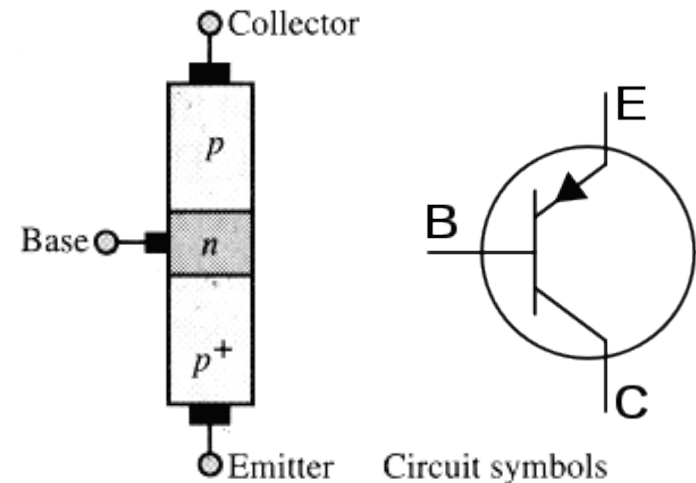

Drive A DC Motor Using An NPN BJT



- How about this?
- Need a kickback diode!!
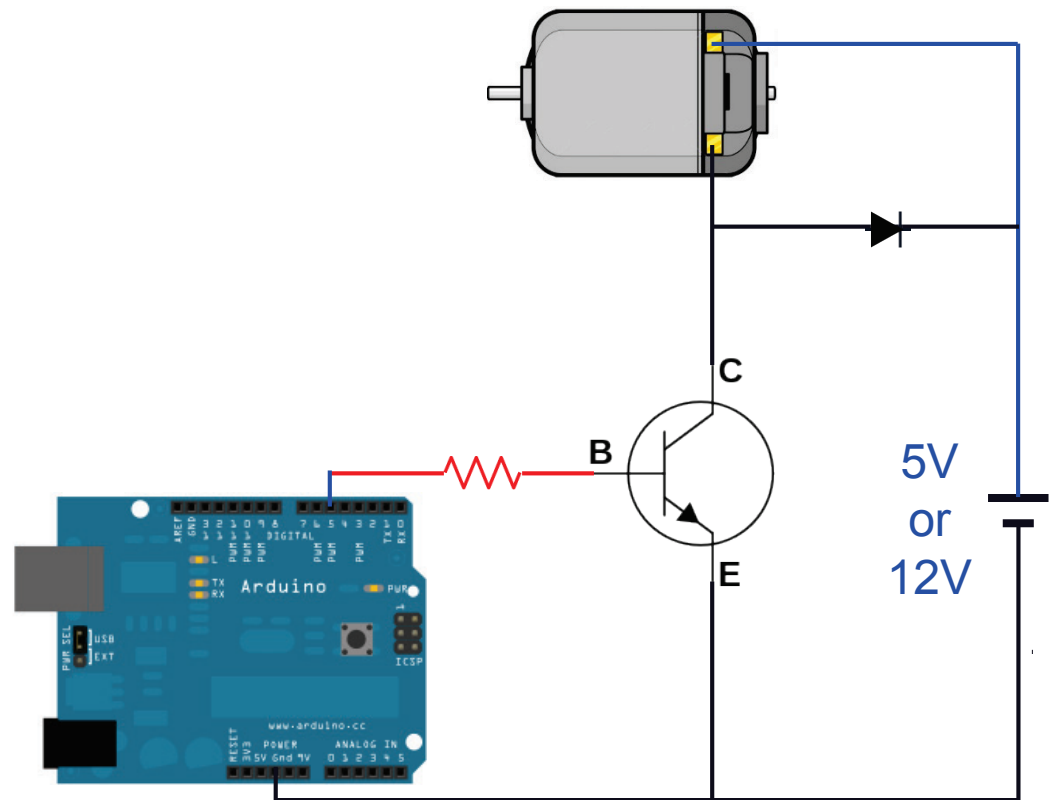
```
int motor = 5;  
void setup() {  
  pinMode(motor, OUTPUT);  
}  
void loop() {  
  digitalWrite(motor, HIGH);  
  delay(4000);  
  digitalWrite(motor, LOW);  
  delay(4000);  
}
```




Kickback Diode

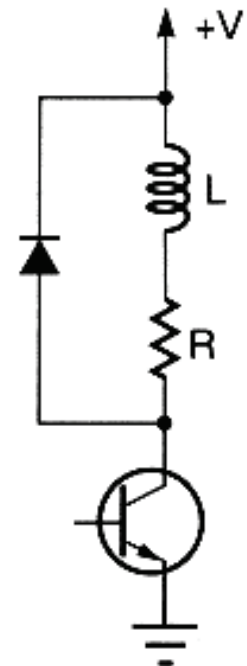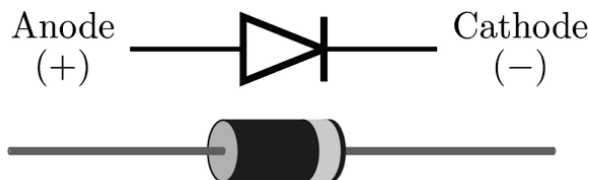- The voltage across an inductor is: $V_{IND} = L \cdot \frac{di_{IND}}{dt}$
- A large voltage will build-up across the inductor at the moment of switch-off
- This voltage can be large enough to damage the transistor
- To avoid this, a freewheeling (kickback) diode can be added in parallel with the inductive load:




H-bridge Motor Drivers

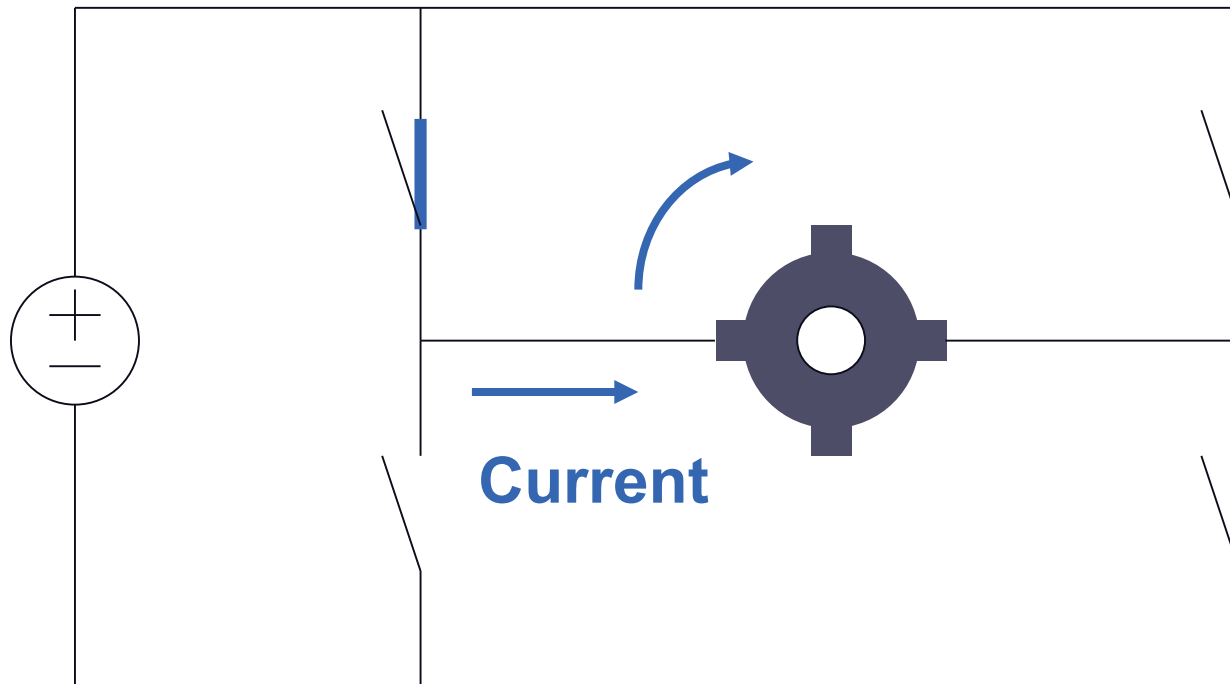- Built with four switches that enable a voltage to be applied across a load in either direction
- One switch is closed in each leg of the "H"




H-bridge Motor Driver (Cont'd)

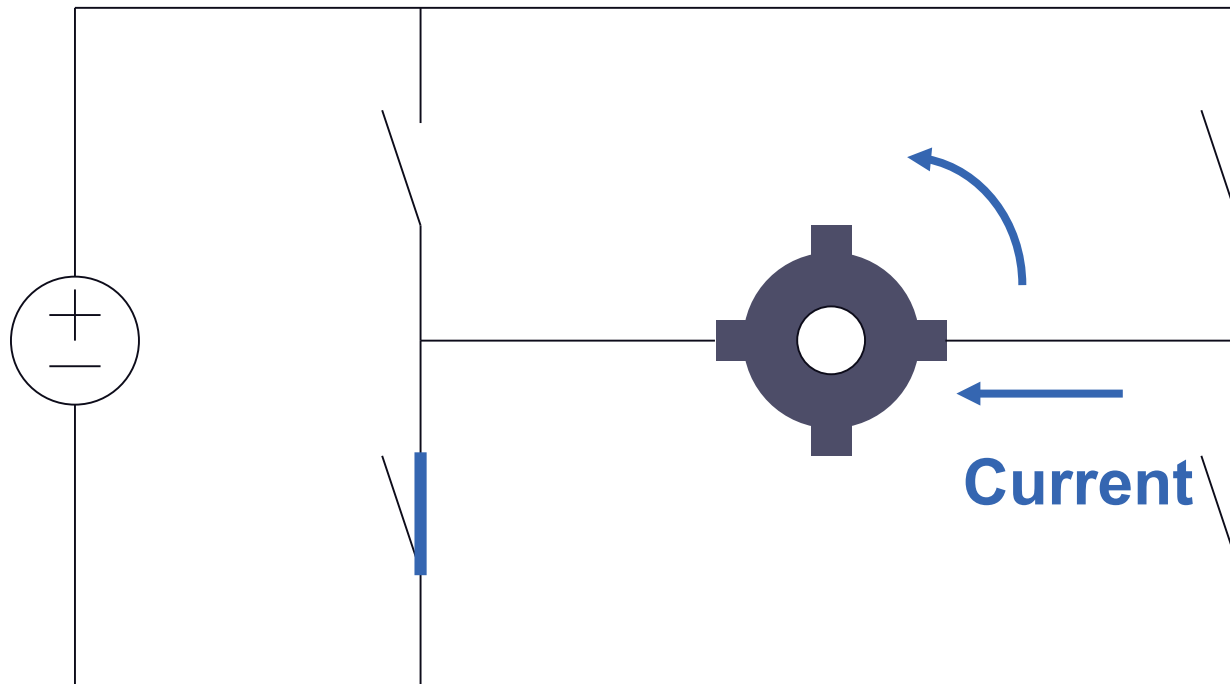- Built with four switches that enable a voltage to be applied across a load in either direction
- One switch is closed in each leg of the "H"





Motor Drivers – H-bridge (Cont'd)

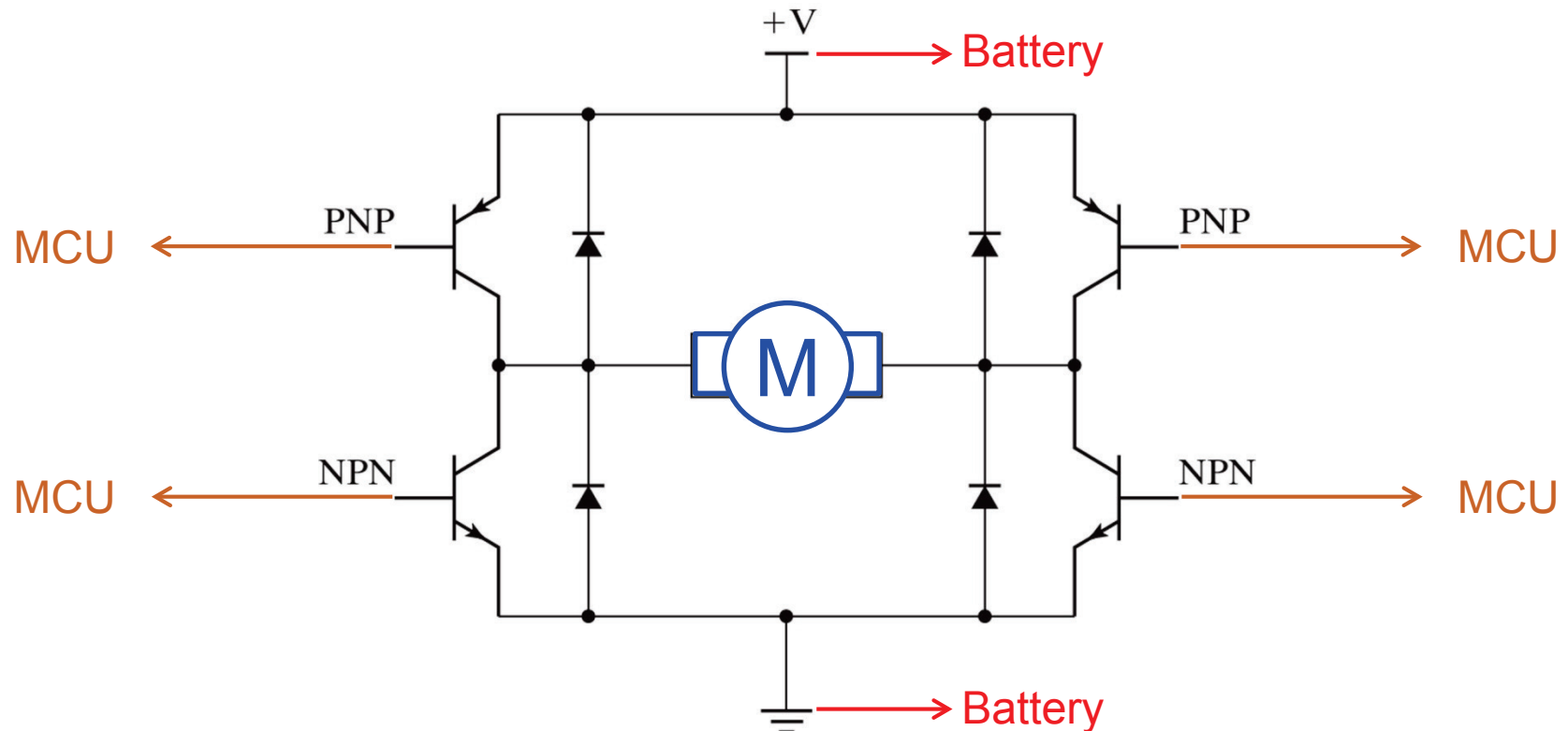- H-bridge – 4 transistors arranged in two 'push-pull' pairs
- Allows current to flow through the motor in either direction with a single-polarity power supply



L298 Dual H-bridge Board

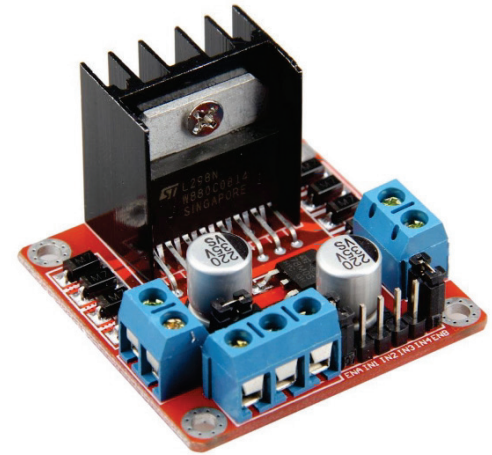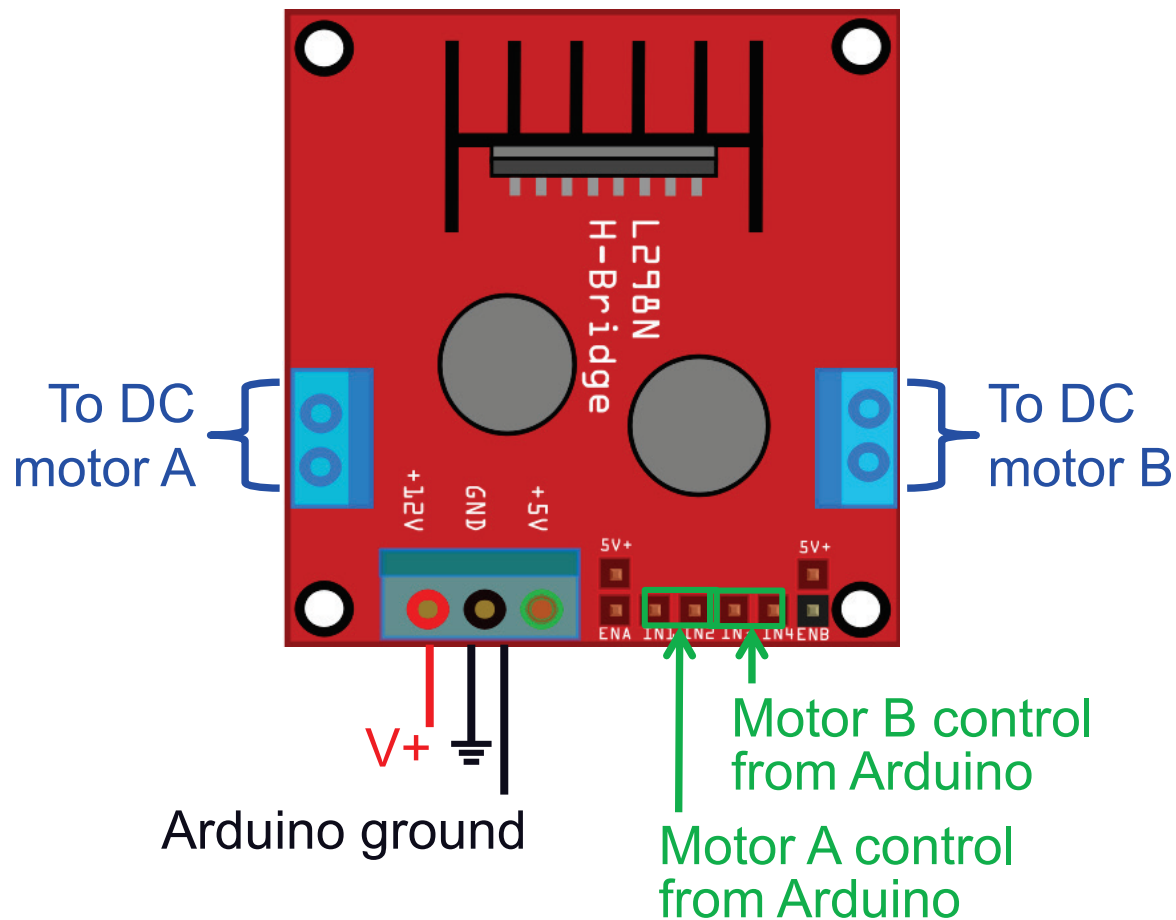


IN1	IN2	Motor A
1	0	CW
0	1	CCW

IN3	IN4	Motor B
1	0	CW
0	1	CCW

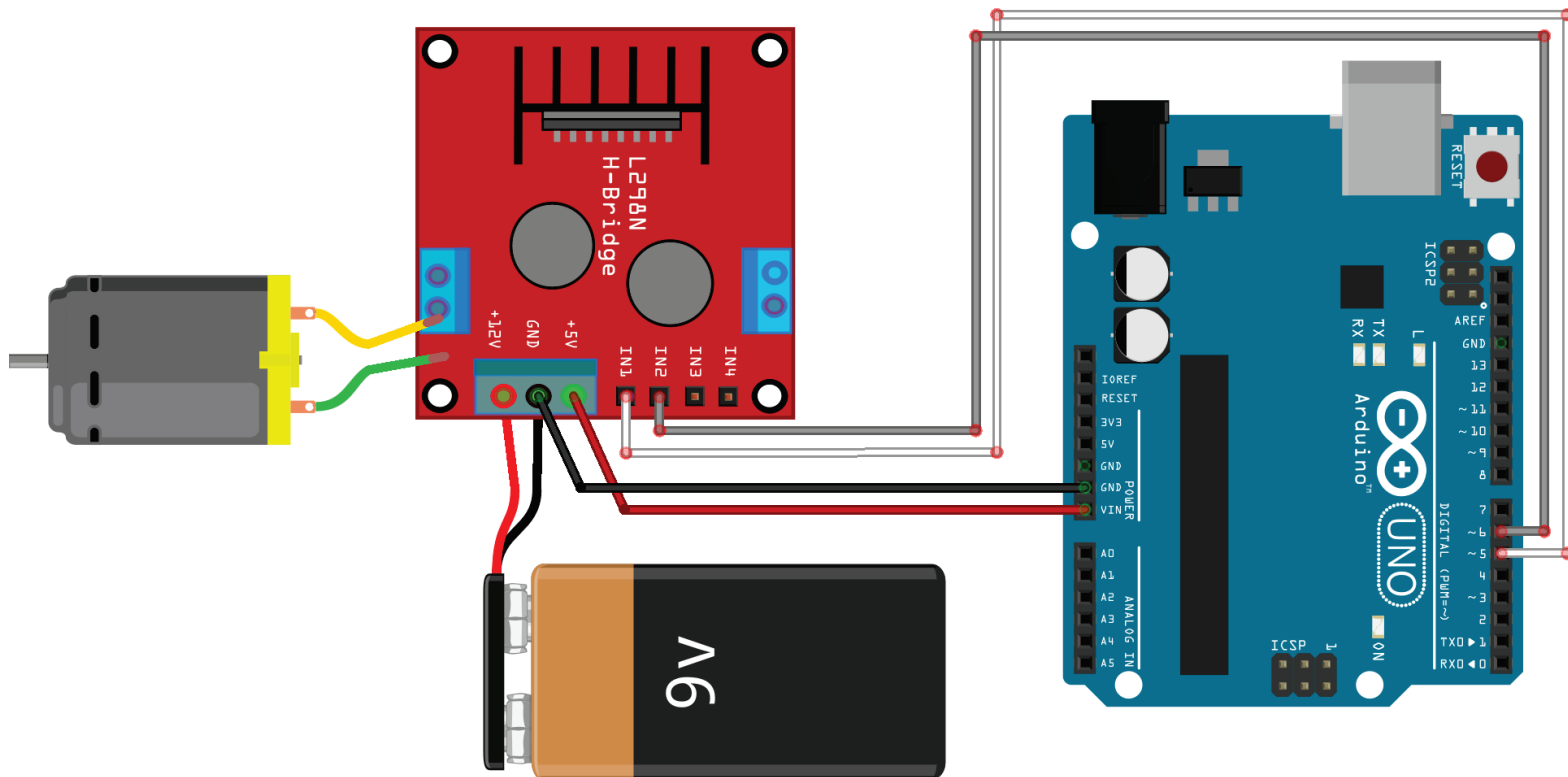Example – DC Motor

- Rotate a DC motor clockwise and counter-clockwise back and forth
- Remember to wire Arduino ground to the H-bridge ground








Sketch Code – DC Motor

```
void setup() {  
  pinMode(5, OUTPUT);  
  pinMode(6, OUTPUT);  
}  
  
void loop() {  
  digitalWrite(5, HIGH);  
  digitalWrite(6, LOW);  
  delay(4000);  
  digitalWrite(6, HIGH);  
  digitalWrite(5, LOW);  
  delay(4000);  
}
```

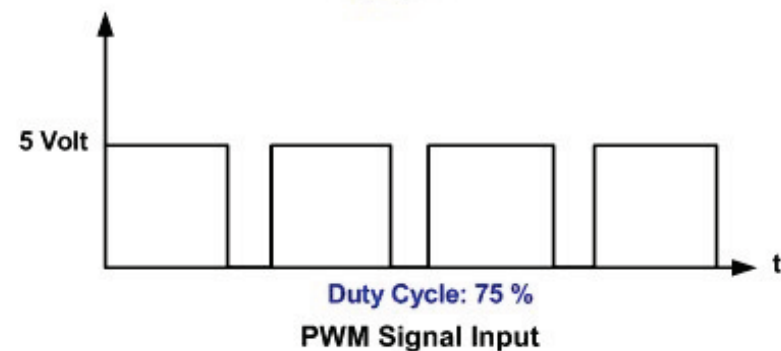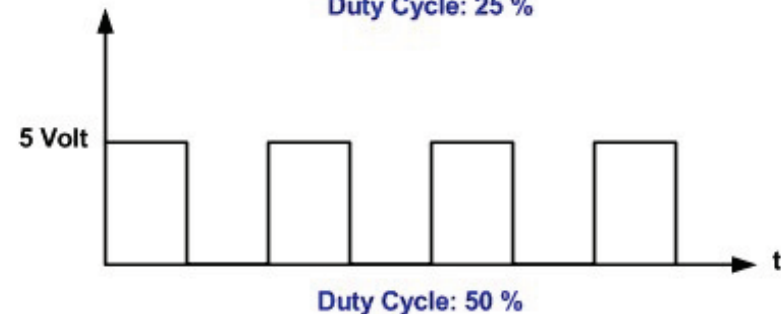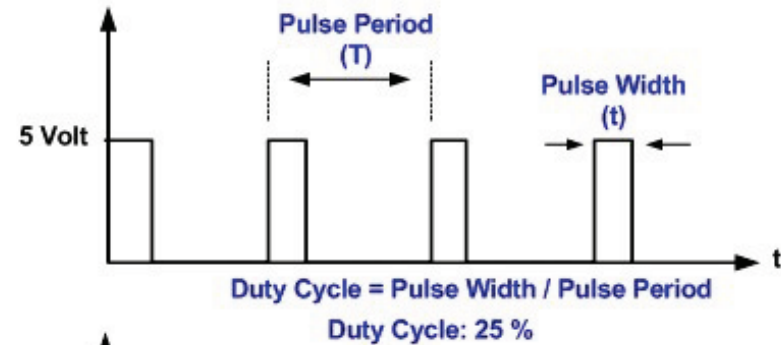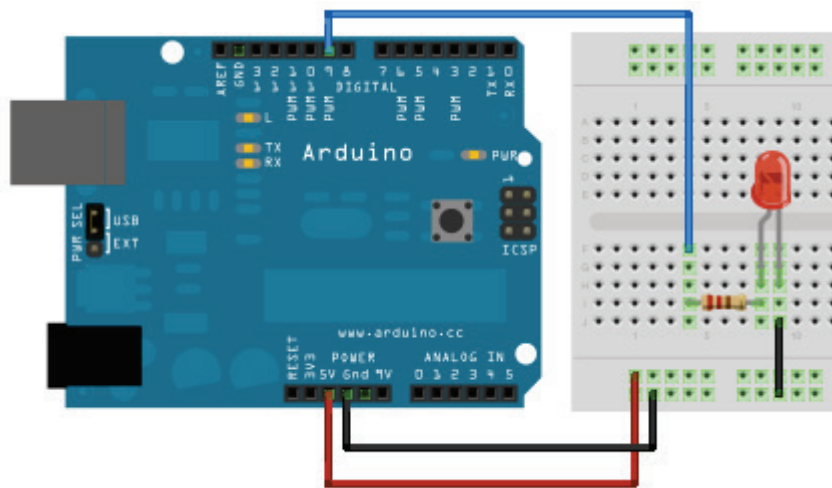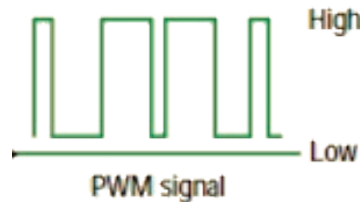Example – Fading

- Fade an LED off and on with pulse width modulation (PWM)
- PWM signals are square waves about 490Hz



Sketch Code – Fading

```
int ledPin = 9;  // LED connected to digital pin 9

void setup() {
}

void loop() {
  // fade in from min to max in increments of 5 points:
  for (int fadeValue = 0 ; fadeValue <= 255; fadeValue += 5) {
    analogWrite(ledPin, fadeValue);
    delay(30); // wait for 30 milliseconds to see the dimming effect
  }
  // fade out from max to min in increments of 5 points:
  for (int fadeValue = 255 ; fadeValue >= 0; fadeValue -= 5) {
    analogWrite(ledPin, fadeValue);
    delay(30); // wait for 30 milliseconds to see the dimming effect
  }
}
```

What are the minimum and maximum `analogWrite` values?

What Have We Learned So Far?

- BJT transistors can be used as a switch
- DC motors are usually driven using H-bridges
- Kickback diodes are used to prevent damages caused by switch-off current introduced by an inductor
- There is an approach to output pseudo analog signals using digital outputs - PWM

Getting Started



Reference

- <http://www.arduino.cc/>
- ATmega328P data sheet